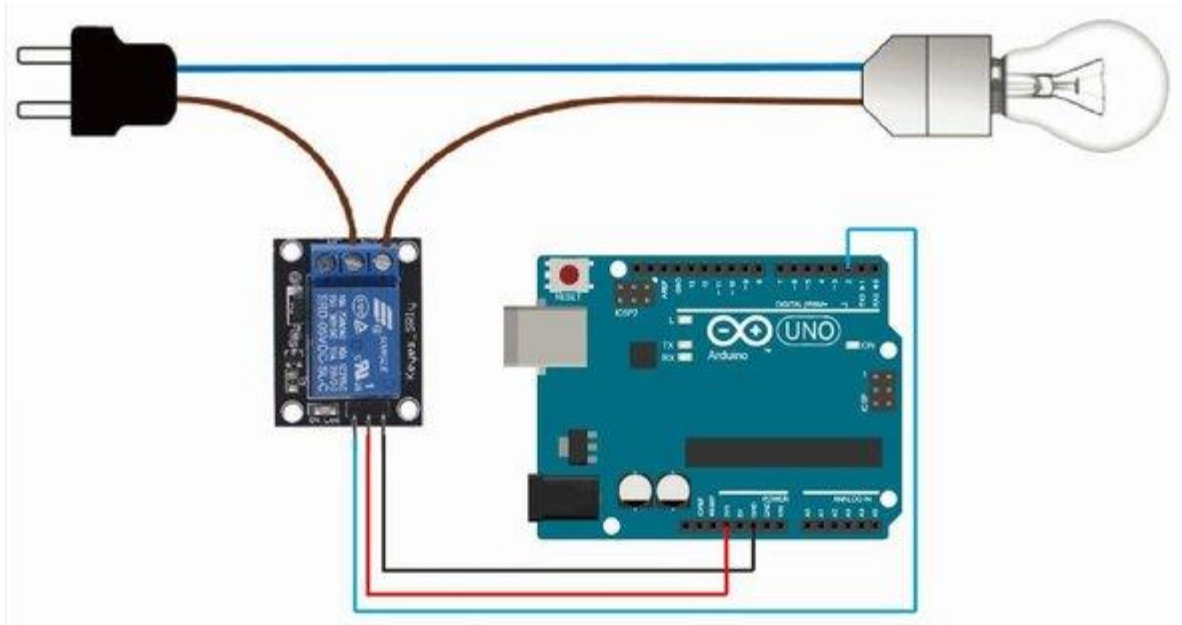


PRAKTIKUM 10

Wiring :



UNO	Relay
5v	VCC
GND	GND
2	OUT

Code :

```
void setup() {  
  pinMode(2, OUTPUT);  
}  
void loop() {  
  digitalWrite(2, HIGH);  
  delay(1000);  
  digitalWrite(2, LOW);  
  delay(1000); }  
}
```